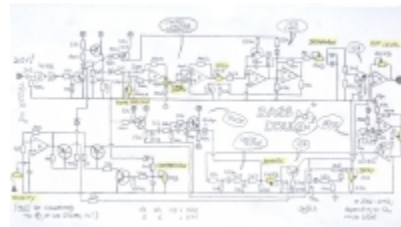


JS Synths Index

On this page you will find all you need for building your own tr909 bass drum circuit (PCB, schematic, component placement).

As an addition to these modifications, I added a "compression" pot, changing the behaviour of the envelope of the tri/sine signal a bit, see schematics for detail. As it is a standalone bass drum, I added the noise circuit on the board. Noise is adjustable from 0% to maximum, unlike in the original TR909.

Schematic, klick on the thumbnail to get the high resolution image.



This is how two of these circuits fit into my MOD2...



...and of course, [how it sounds. As you can hear, the PCB works fine.](#) (in this case, I triggered the two 909-bass drums with my [16 step trigger sequencer.](#))